

## Prelab 3

### Part 0 – Preparation for the Lab

1. What one thing and one thing only will you stick into the 14-pin connectors on the boards?

I will ribbon cables only to the 14-pin connectors on the board.

2. Draw a detailed state diagram for a hypothetical software PWM driver. Include an example plot of the expected output signal for a given frequency and duty cycle.

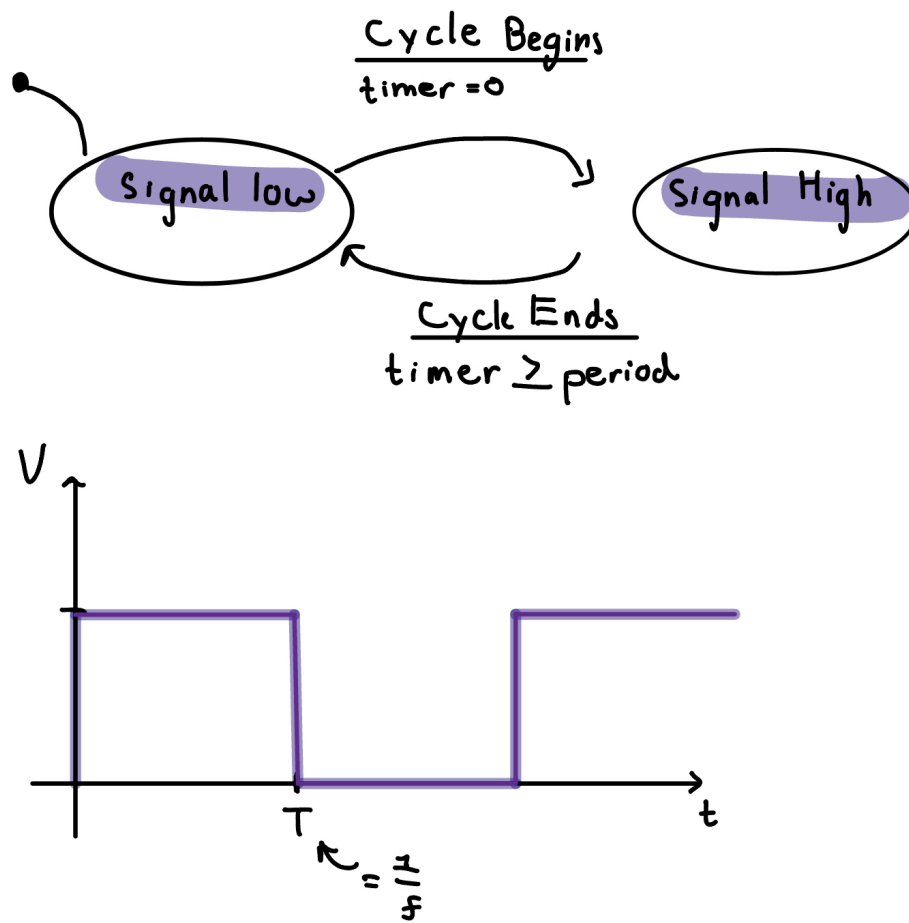


Figure 1:

## Part 1 – Driving an RC Servo

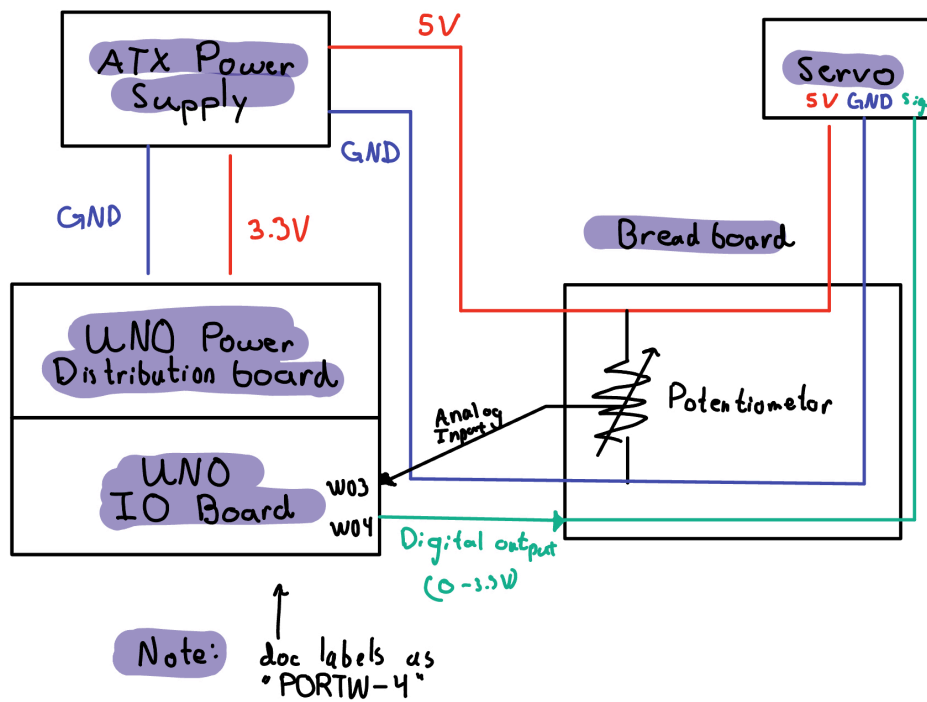


Figure 2:

## Part 2 – Unidirectional Drive of a DC Motor

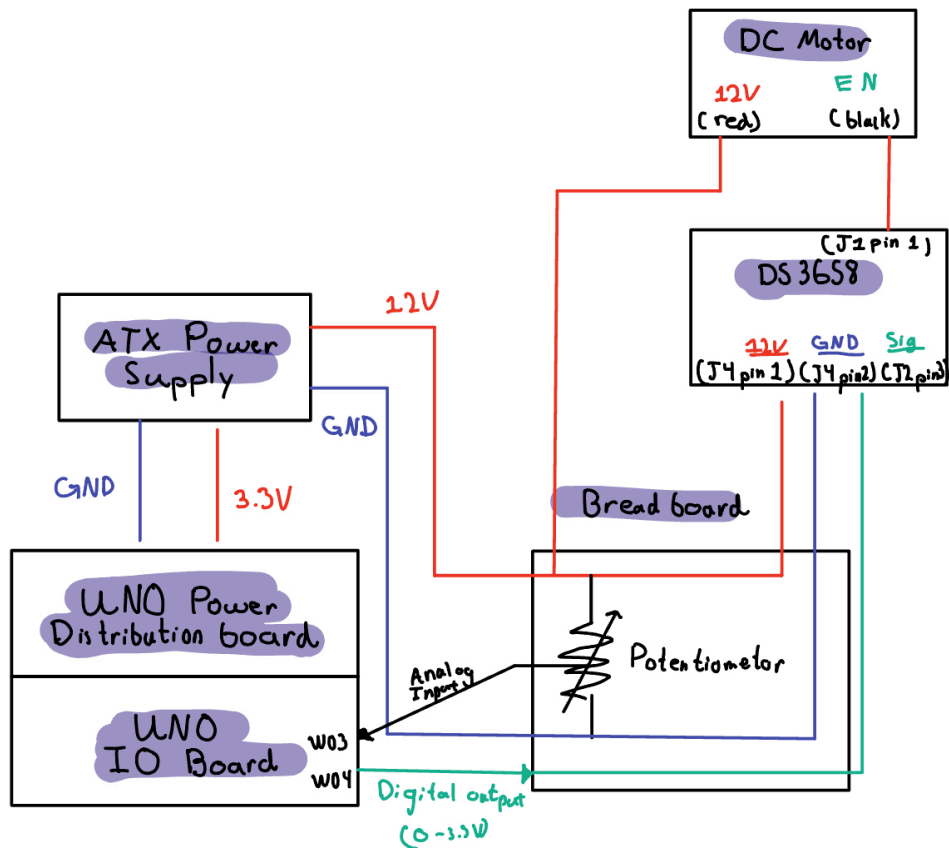


Figure 3:

```
int main() {  
  // ...  
}
```

```

// Initialization Section
AD_Init();
PWM_Init();
RC_Init();

// Specify Pin Usage:
AD_AddPins(AD_PORTV3|AD_PORTV4);
RC_AddPins(RC_PORTX03|RC_PORTX04);

// ...
}

```

### Part 3 – Snubbing the Inductive Kickback

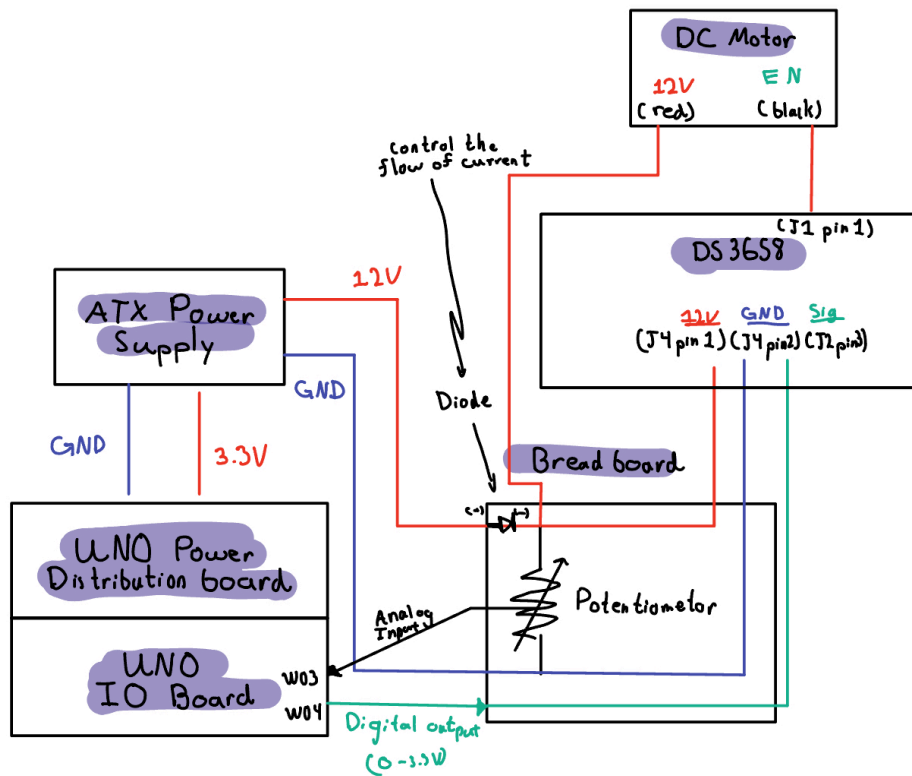


Figure 4:

## Part 4 – Bidirectional Control of a DC Motor

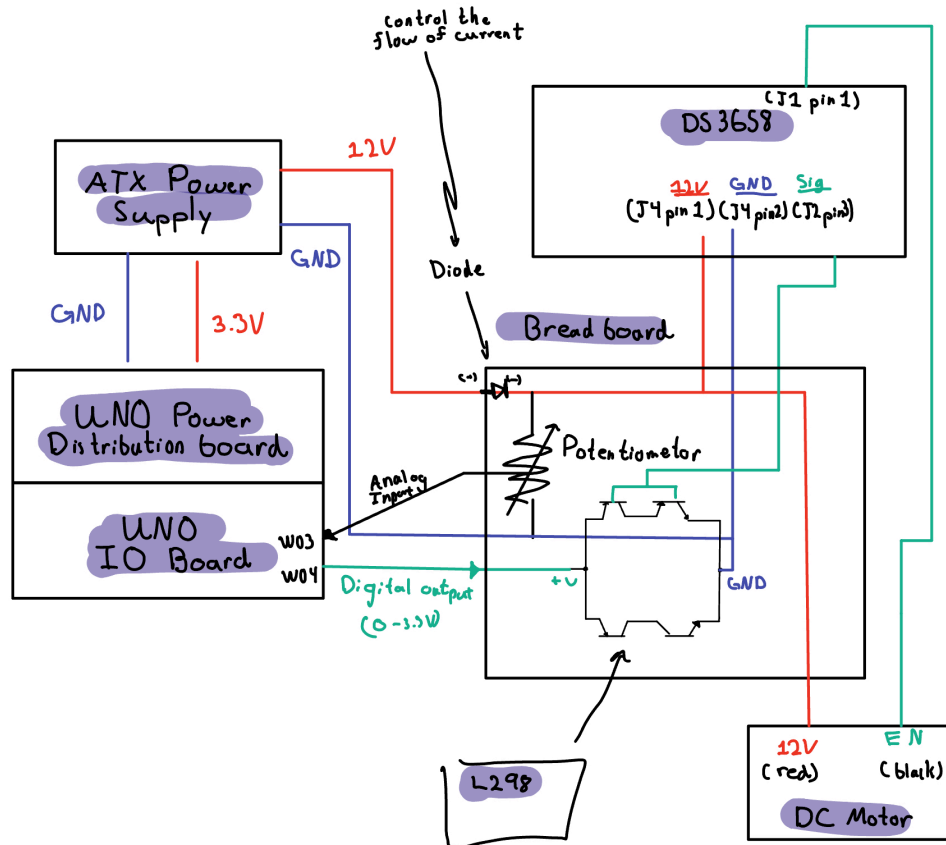


Figure 5:

```
int main() {  
    // ...  
  
    // Initialization Section  
    AD_Init();  
    PWM_Init();  
    RC_Init();  
  
    // Specify Pin Usage:  
    AD_AddPins(AD_PORTV3|AD_PORTV4);  
    RC_AddPins(RC_PORTX04|RC_PORTX05);  
  
    // ...  
}
```

## Part 5 – Control of a Stepper Motor

**Note:** The Arrows are determined by the step which is either counter-clockwise or clockwise

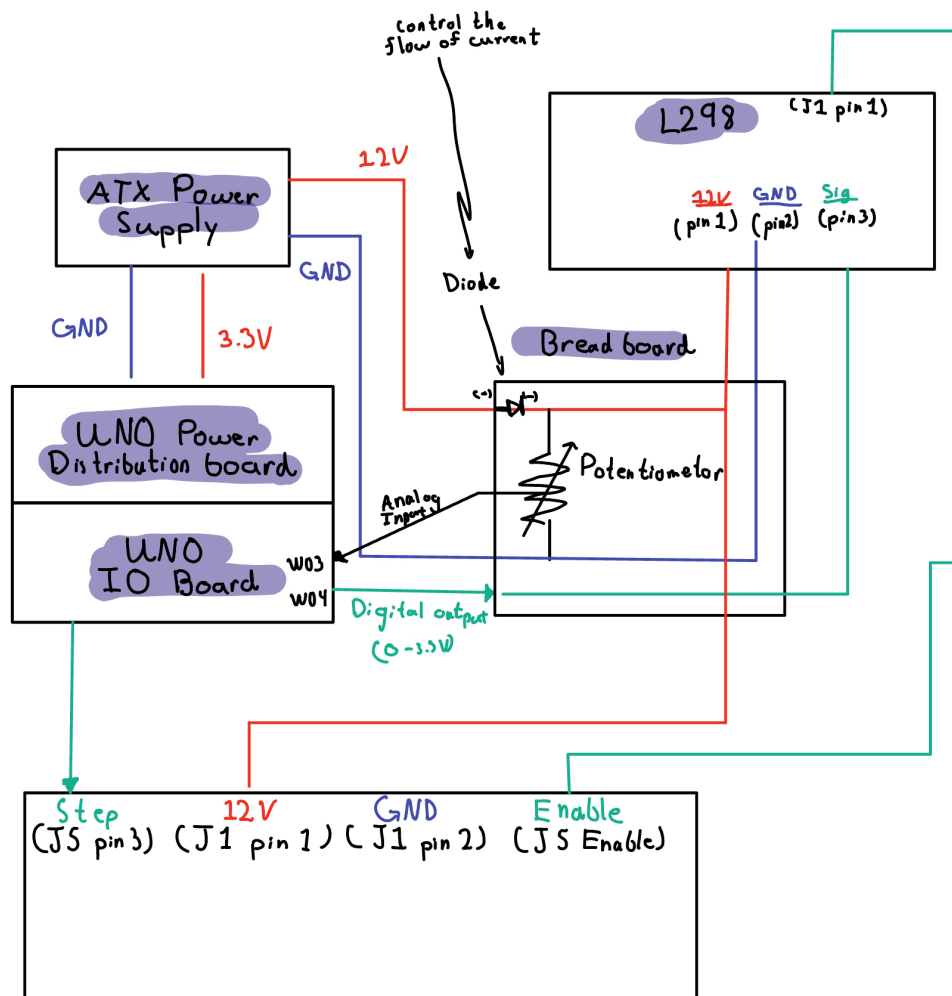


Figure 6:

### Full Step Mode:


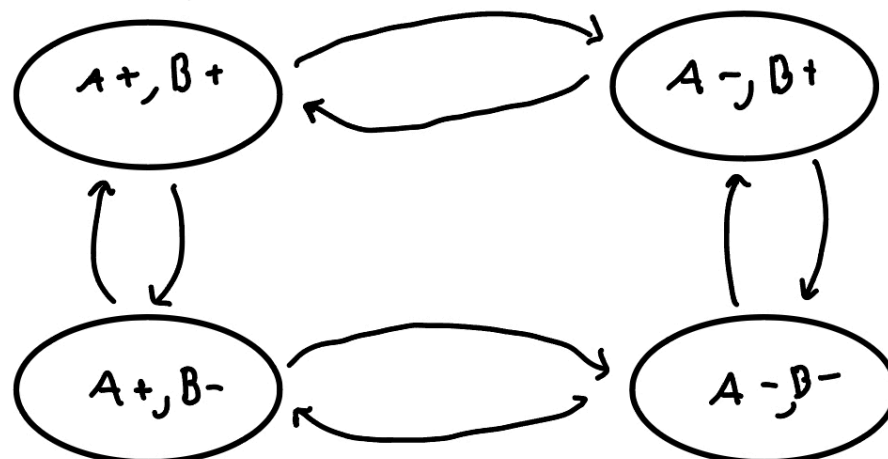


Figure 7:

### Half Step Mode:

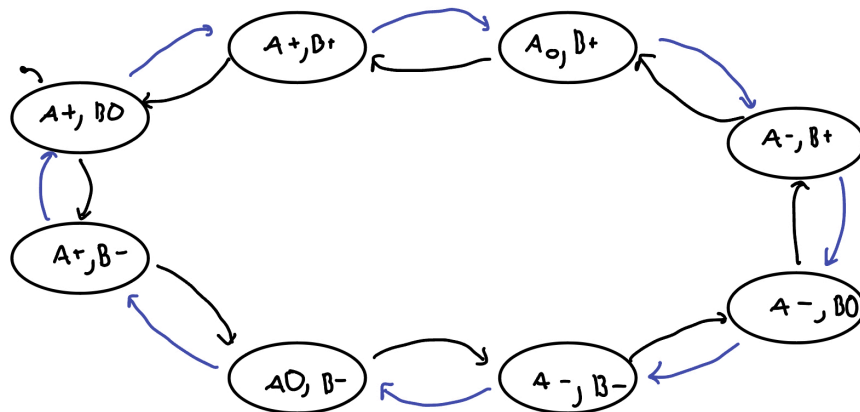

\* Every change in 1 direction or another on each clk cycle.  
 \* Blue = clockwise , white = counterclockwise

Figure 8:

### Wave Mode:

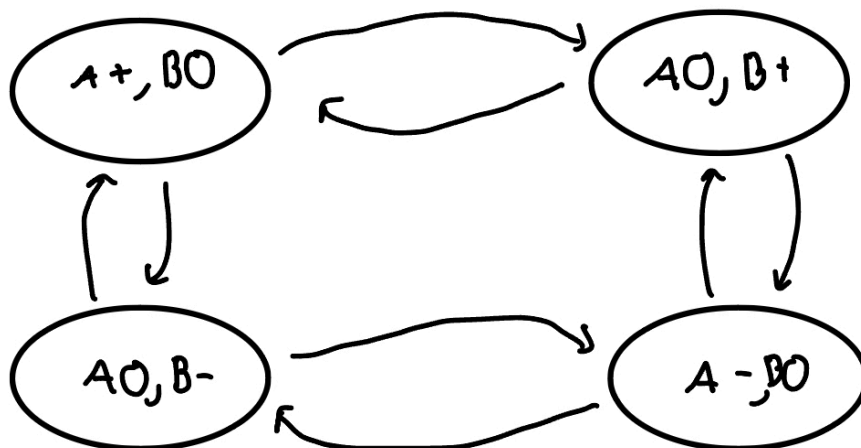


Figure 9:

Coil Polarity	Binary Value
A+ (positive)	10
A0 (not energized)	00
A- (negative)	01
B+ (positive)	10
B0 (not energized)	00
B- (negative)	01

```
int main() {
  // ...
}
```

## Part 6 – Stepper Motor using Dedicated Board



```
int main() {
    // ...

    // Initialization Section
    AD_Init();
    LED_Init();
    PWM_Init();
    RC_Init();
    HSM_Init();

    // Specify Pin Usage:
    AD_AddPins(AD_PORTV3|AD_PORTV4);
}
```

```
RC_AddPins(RC_PORTX03|RC_PORTX04|RC_PORTX05);  
  
// ...  
}
```